

Date:

EXPERIMENT NO. 5**AIM:** Design, Implement and verify operation of 2-bit magnitude comparator circuit.**APPARATUS:** connection wires, power supply, power project board, resistors, LED, ICs

Sr.No.	Component	Specification	Quantity
1	AND Gate	IC 7408	1
2	OR Gate	IC 7432	1
3	NOT Gate	IC 7404	1
4	XOR Gate	IC7486	1
5	Three input AND Gate	IC7411	1

SIMULATION WEBSITE: <https://www.tinkercad.com/>**THEORY:****Definition**


A magnitude comparator is a combinational circuit that compares two numbers **A** & **B** to determine whether:

- **A** > **B**, or
- **A** = **B**, or
- **A** < **B**

InputsFirst **n**-bit number **A**Second **n**-bit number **B****Outputs**

3 output signals (GT, EQ, LT), where:

1. **GT** = 1 **IFF** **A** > **B**
2. **EQ** = 1 **IFF** **A** = **B**
3. **LT** = 1 **IFF** **A** < **B**

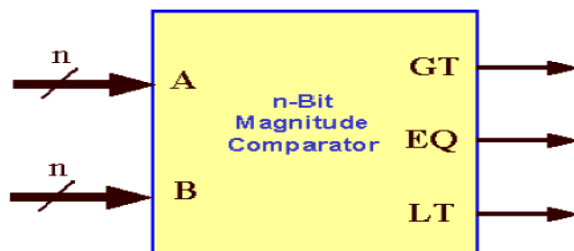Note: Exactly One of these 3 outputs equals 1, while the other 2 outputs are 0's**4-bit magnitude comparator****Inputs:** 8-bits (**A** ⇒ 4-bits, **B** ⇒ 4-bits)**A** and **B** are two 4-bit numbers

- Let **A** = **A**₃**A**₂**A**₁**A**₀, and
- Let **B** = **B**₃**B**₂**B**₁**B**₀
- Inputs have 2⁸ (256) possible combinations
- Not easy to design using conventional techniques


2-Bit Magnitude Comparator:

A comparator used to compare two binary numbers each of two bits is called a 2-bit Magnitude comparator. It consists of four inputs and three outputs to generate less than, equal to, and greater than between two binary numbers.

The truth table for a 2-bit comparator is given below:

INPUT				OUTPUT		
A1	A0	B1	B0	A<B	A=B	A>B
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	1	0	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	0	1

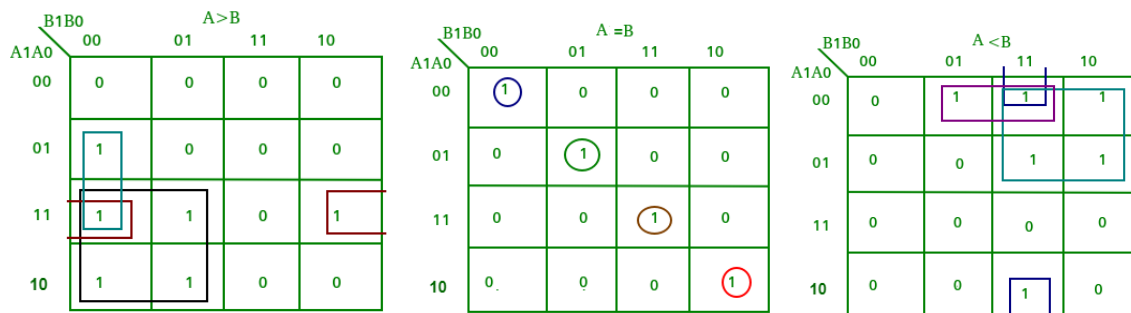From the above truth table K-map for each output can be drawn as follows:



$$A>B: A1B1' + A0B1'B0' + A1A0B0'$$

$$A=B: A1'A0'B1'B0' + A1'A0B1'B0 + A1A0B1B0 + A1A0'B1B0'$$


$$: A1'B1' (A0'B0' + A0B0) + A1B1 (A0B0 + A0'B0')$$

$$: (A0B0 + A0'B0') (A1B1 + A1'B1')$$

$$: (A0 \text{ Ex-Nor } B0) (A1 \text{ Ex-Nor } B1)$$

$$A<B: A1'B1 + A0'B1B0 + A1'A0'B0$$


By using these Boolean expressions, we can implement a logic circuit for this comparator as given below:

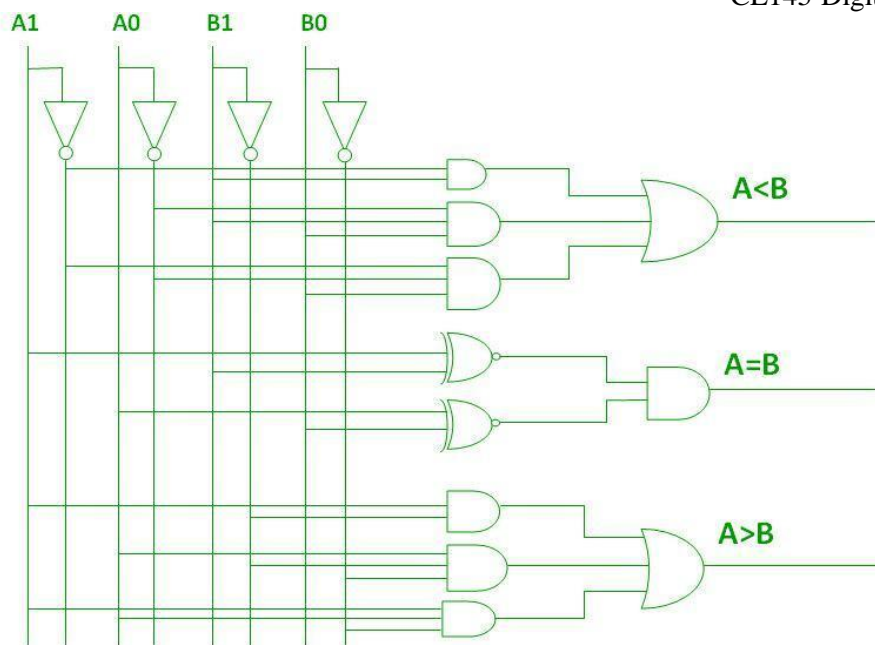**PROCEDURE:**

- Make connections as per logic circuit diagram.
- Apply proper input condition and observe the output information of led on/off.
- Apply all possible combinations of input and verify correctness of circuit output as per truth tables.

OBSERVATION TABLE:


Serial No.	A ₁	A ₀	B ₁	B ₀	A > B	A = B	A < B
1	0	0	0	0	0	1	0
2	0	0	0	1	0	0	1
3	0	0	1	0	0	0	1
4	0	0	1	1	0	0	1
5	0	1	0	0	1	0	0
6	0	1	1	0	0	0	1
7	0	1	1	1	0	0	1
8	1	0	0	0	1	0	0

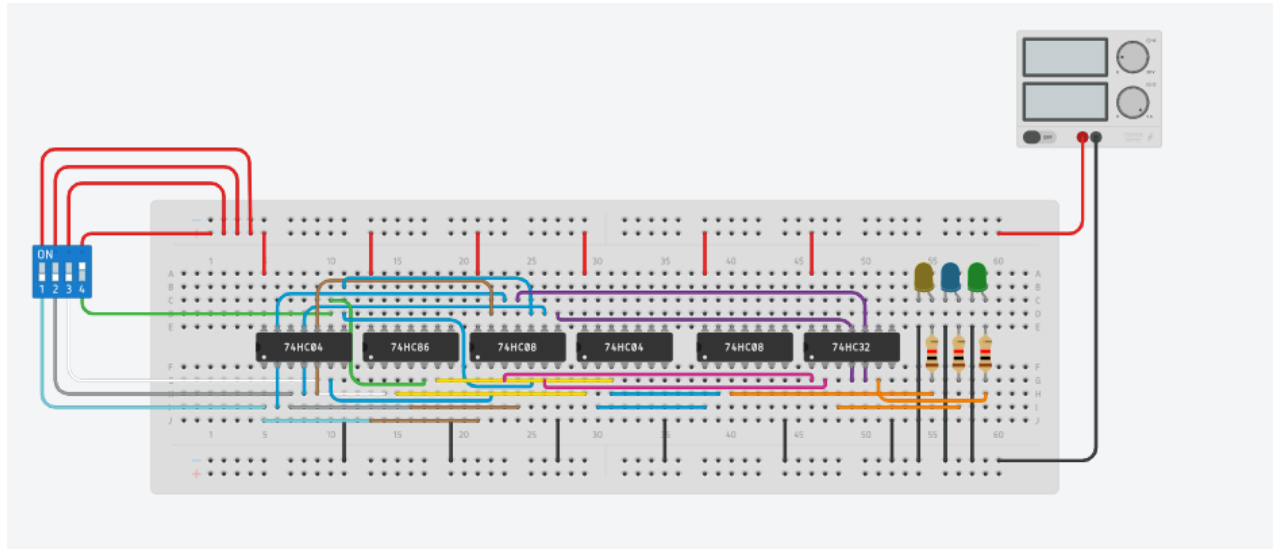OBSERVATION:**Obtained Marks:****Faculty Sign:****Date:****ASSIGNMENT:**


1. Simulate 1 bit and 2-bit magnitude comparator experiment on <http://vlabs.iitb.ac.in/vlabs-dev/labs/digital-electronics/experiments/verify-truth-table-of-one-bit-and-two-bit-comparator-iitr/simulation.html> and show results.

Ans.

1-bit magnitude comparator:

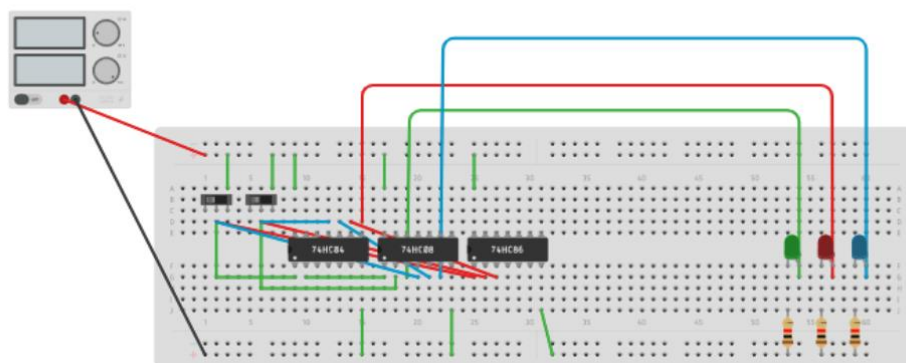

2-bit magnitude comparator:

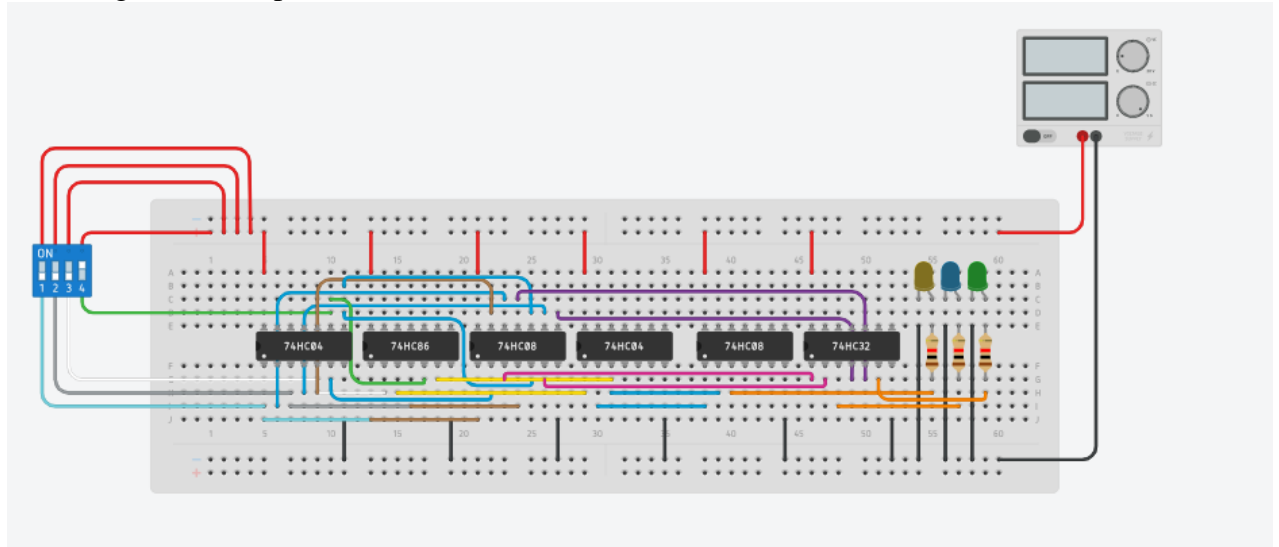

2. Draw pin diagram of IC 7485 and explain how it can be used for 4 bit magnitude comparison.
Ans.

