

## Unit 1

# Register Transfer and Microoperations

# Contents

- **Register Transfer Language**
- **Register Transfer**
- **Bus and Memory Transfers**
- **Arithmetic Microoperations**
- **Logic Microoperations**
- **Shift Microoperations**
- **Arithmetic Logic Shift Unit**


# 1-1 Register Transfer Language (RTL)

- **Digital System:** An interconnection of hardware modules that do a certain task on the information.
- Registers + Operations performed on the data stored in them = **Digital Module**
- Modules are interconnected with common data and control paths to form a digital computer system
 
# 1-1 Register Transfer Language

cont.

- **Microoperations:** operations executed on data stored in one or more registers.
- For any function of the computer, a sequence of microoperations is used to describe it
- The result of the operation may be:
  - replace the previous binary information of a register or
  - transferred to another register



# 1-1 Register Transfer Language

cont.

- The internal hardware organization of a digital computer is defined by specifying:
  - The **set of registers** it contains and their function
  - The **sequence of microoperations** performed on the binary information stored in the registers
  - The **control** that initiates the sequence of microoperations
- **Registers + Microoperations Hardware + Control Functions = Digital Computer**


# 1-1 Register Transfer Language

cont.

- Register Transfer Language (RTL) : a symbolic notation to describe the microoperation transfers among registers


Next steps:

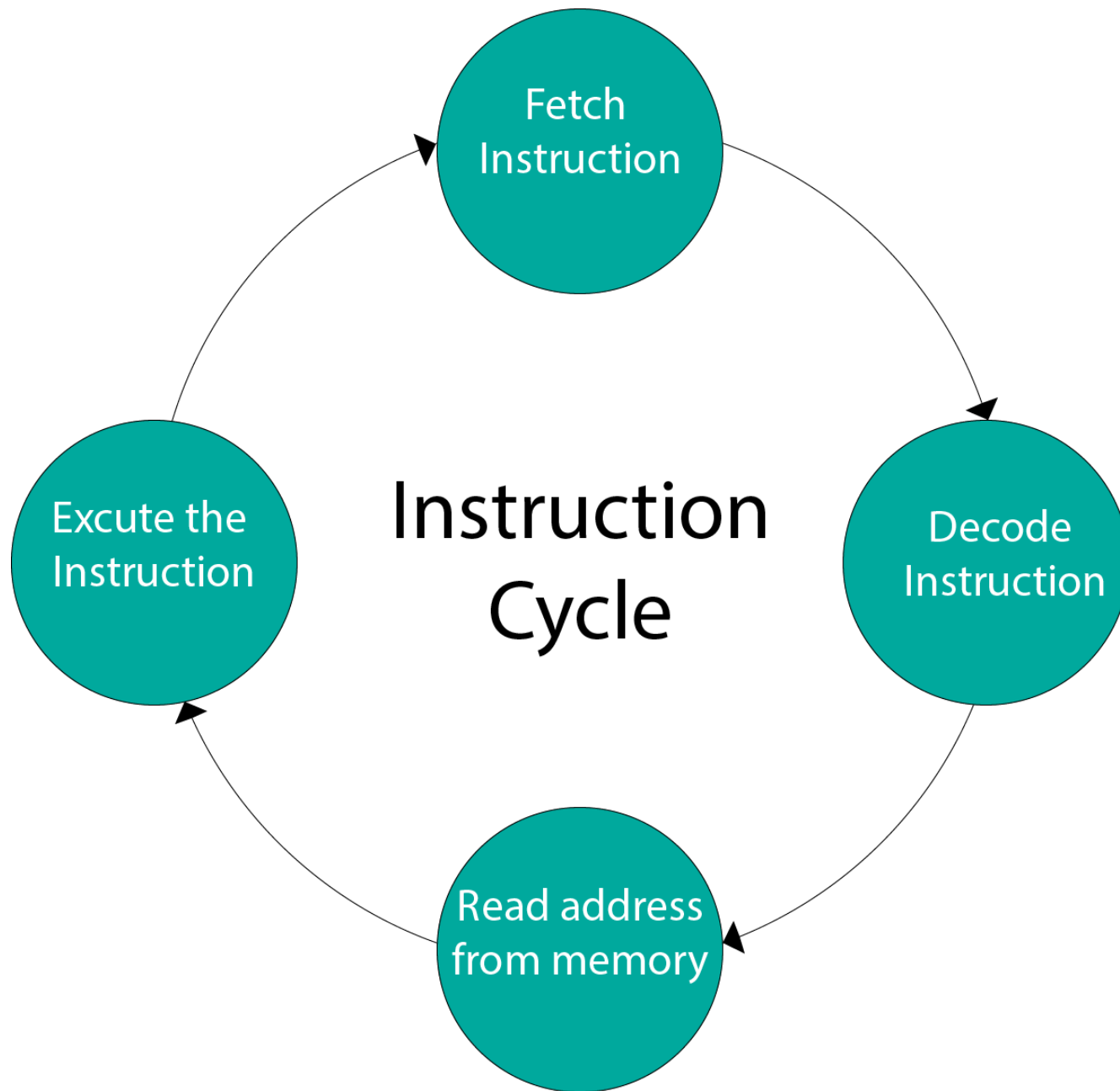- Define symbols for various types of microoperations,
- Describe the hardware that implements these microoperations


 
# 1-2 Register Transfer (our first microoperation)


- Computer registers are designated by capital letters (sometimes followed by numerals) to denote the function of the register
  - R1: processor register
  - MAR: Memory Address Register (holds an address for a memory unit)
  - PC: Program Counter (each instruction gets fetched, the **program counter** increases its stored value by 1)
  - IR: Instruction Register (that holds the **instruction** currently being executed or decoded)
  - SR: Status Register





 
# 1-2 Register Transfer <sup>cont.</sup>

- The individual flip-flops in an n-bit register are numbered in sequence from 0 to n-1 **(from the right position toward the left position)**



Register R1

 


Showing individual bits


**A block diagram of a register**
 
# 1-2 Register Transfer cont.

Other ways of drawing the block diagram of a register:



Numbering of bits

 

Partitioned into two parts

# 1-2 Register Transfer cont.

- Information transfer from one register to another is described by a *replacement operator*:  $R2 \leftarrow R1$
- This statement denotes a transfer of the content of register R1 into register R2
- **The transfer happens in one clock cycle**
- The content of the R1 (source) does not change
- The content of the R2 (destination) will be lost and replaced by the new data transferred from R1
- We are assuming that the circuits are available from the outputs of the source register to the inputs of the destination register, and that the destination register has a parallel load capability


# 1-2 Register Transfer <sup>cont.</sup>

- Conditional transfer occurs only under a control condition
- Representation of a (conditional) transfer  
P:       $R2 \leftarrow R1$
- A binary condition (P equals to 0 or 1) determines when the transfer occurs
- The content of R1 is transferred into R2 only if P is 1


# 1-2 Register Transfer cont.

Hardware implementation of a controlled transfer:  $P: R2 \leftarrow R1$

**Block diagram:**

 

**Timing diagram**

 


# 1-2 Register Transfer cont.

Basic Symbols for Register Transfers		
Symbol	Description	Examples
Letters & numerals	Denotes a register	MAR, R2
Parenthesis ( )	Denotes a part of a register	R2(0-7), R2(L)
Arrow $\leftarrow$	Denotes transfer of information	$R2 \leftarrow R1$
Comma ,	Separates two microoperations	$R2 \leftarrow R1, R1 \leftarrow R2$


# 1-3 Bus and Memory Transfers

- **Paths** must be provided to transfer information from one register to another
- A **Common Bus System** is a scheme for transferring information between registers in a multiple-register configuration
- **A bus:** set of common lines, one for each bit of a register, through which binary information is transferred one at a time
- **Control signals** determine which **register is selected** by the bus during each particular register transfer

# 1-3 Bus and Memory Transfers

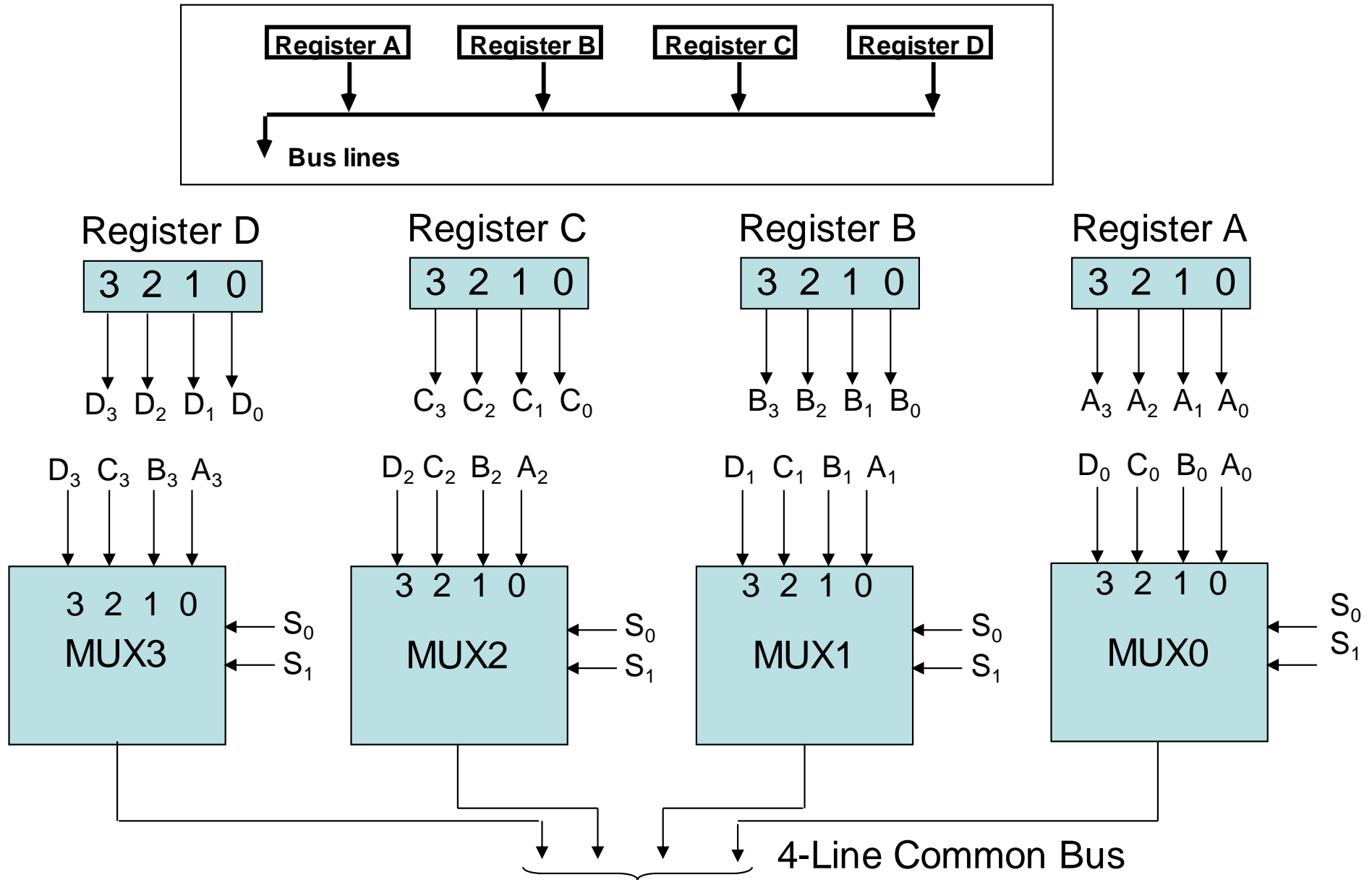



 






# 1-3 Bus and Memory Transfers

- The transfer of information from a bus into one of many destination registers is done:
  - By **connecting the bus lines to the inputs of all destination registers and then:**
  - **activating the load control of the particular destination register selected**
- We write:  $R2 \leftarrow C$  to symbolize that the content of register  $C$  is *loaded into* the register  $R2$  using the common system bus
- It is equivalent to:  $BUS \leftarrow C, (\text{select } C)$   
 $R2 \leftarrow BUS (\text{Load } R2)$


# 1-3 Bus and Memory Transfers:
 
## Three-State Bus Buffers


- A bus system can be constructed with three-state buffer gates instead of multiplexers
- A three-state buffer is a digital circuit that exhibits three states: **logic-0**, **logic-1**, and **high-impedance (Hi-Z)**


 
# 1-3 Bus and Memory Transfers: Three-State Bus Buffers <sup>cont.</sup>


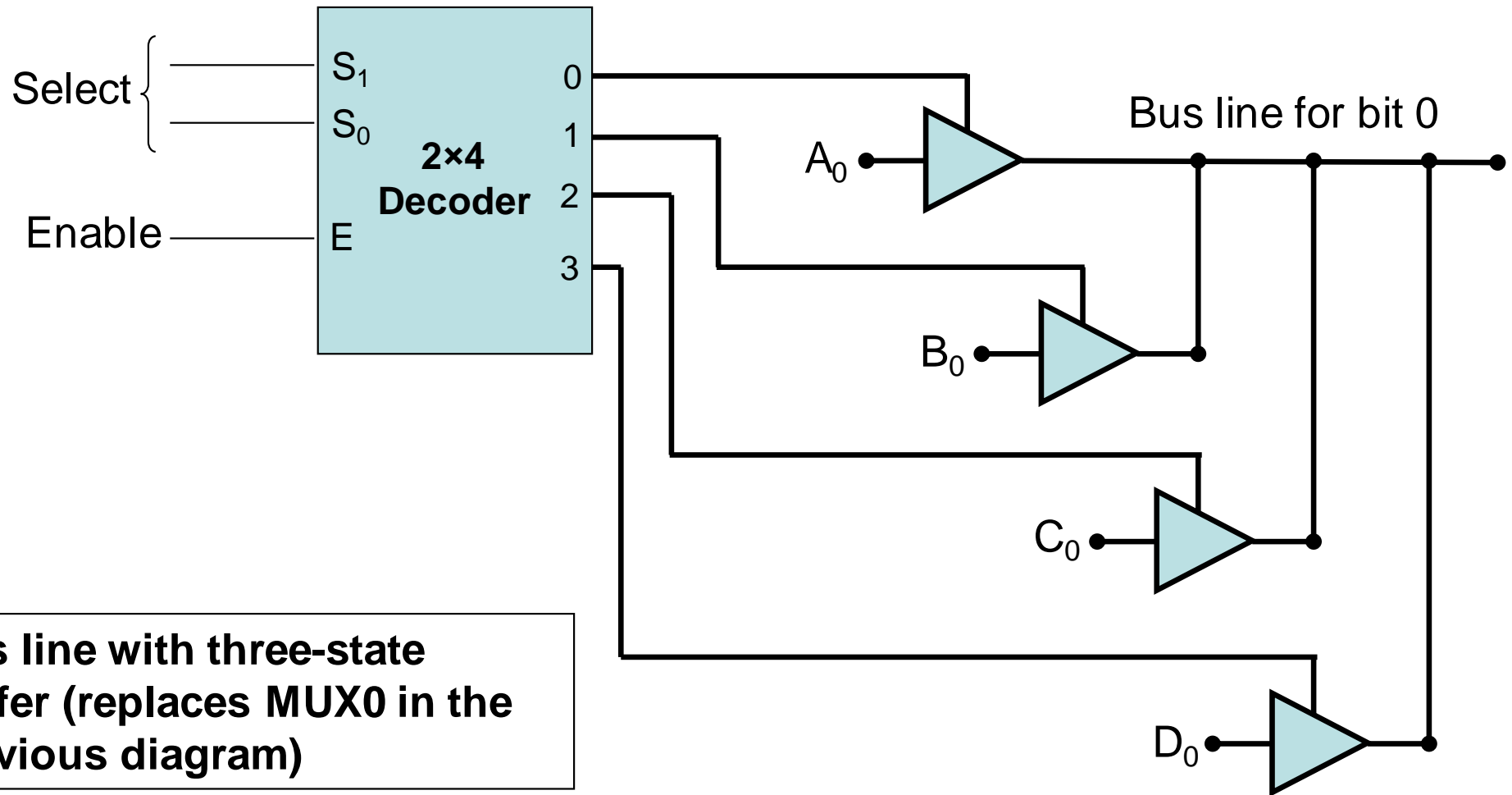
# 1-3 Bus and Memory Transfers: Three-State Bus Buffers <sup>cont.</sup>



# 1-3 Bus and Memory Transfers:

## Memory Transfer

- **Memory read** : Transfer from memory
- **Memory write** : Transfer to memory
- Data being read or wrote is called a **memory word** (called M)
- It is necessary to specify the address of M when writing /reading memory
- This is done by enclosing the address in square brackets following the letter M
- Example: M[0016] : the memory contents at address 0x0016


# 1-3 Bus and Memory Transfers:

## Memory Transfer <sup>cont.</sup>

- Assume that the address of a memory unit is stored in a register called the Address Register **AR**
- Lets represent a Data Register with DR, then:
  - **Read:  $DR \leftarrow M[AR]$**
  - **Write:  $M[AR] \leftarrow DR$**


 
# 1-3 Bus and Memory Transfers: Memory Transfer cont.



# 1-4 Arithmetic Microoperations

- The microoperations most often encountered in digital computers are classified into four categories:
  - **Register transfer microoperations**
  - **Arithmetic microoperations (on numeric data stored in the registers)**
  - **Logic microoperations (bit manipulations on non-numeric data)**
  - **Shift microoperations**

# 1-4 Arithmetic Microoperations cont.

- The basic arithmetic microoperations are:  
**addition, subtraction, increment, decrement, and shift**

- Addition Microoperation:

$$\mathbf{R3 \leftarrow R1 + R2}$$

- Subtraction Microoperation:

$$\mathbf{R3 \leftarrow R1 - R2 \text{ or :}}$$

$$\mathbf{R3 \leftarrow R1 + \overline{R2} + 1}$$

1's complement

# 1-4 Arithmetic Microoperations cont.

- One's Complement Microoperation:

$$\mathbf{R2 \leftarrow \overline{R2}}$$

- Two's Complement Microoperation:

$$\mathbf{R2 \leftarrow \overline{R2} + 1}$$

- Increment Microoperation:

$$\mathbf{R2 \leftarrow R2 + 1}$$

- Decrement Microoperation:

$$\mathbf{R2 \leftarrow R2 - 1}$$

# Half Adder/Full Adder


## Half Adder

x	y	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$c = xy$$



$$s = xy' + x'y$$

$$= x \oplus y$$

 

## Full Adder

x	y	$C_{n-1}$	$C_n$	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

  


$$C_n = xy + xC_{n-1} + yC_{n-1}$$

$$= xy + (x \oplus y)C_{n-1}$$


$$s = x'y'C_{n-1} + x'yc'_{n-1} + xy'c'_{n-1} + xyc_{n-1}$$
 
$$= x \oplus y \oplus C_{n-1} = (x \oplus y) \oplus C_{n-1}$$



# 1-4 Arithmetic Microoperations


## Binary Adder

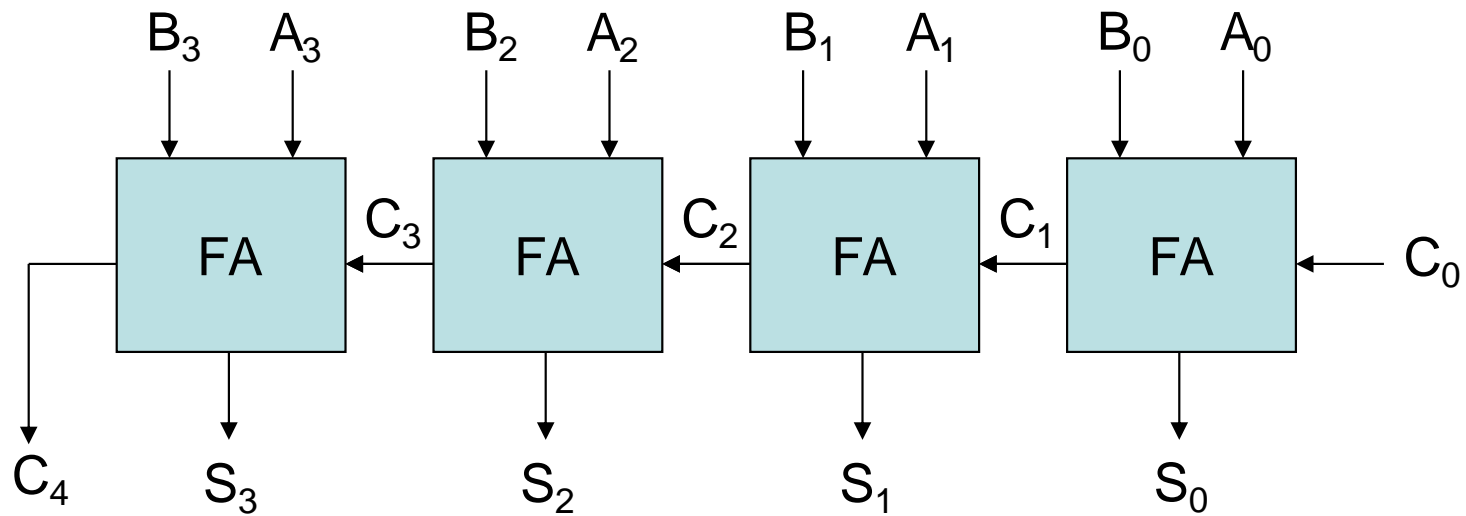

**4-bit binary adder  
(connection of FAs)**

# 1-4 Arithmetic Microoperations


## Binary Adder-Subtractor

 

**4-bit adder-subtractor**

# 1-4 Arithmetic Microoperations

## Binary Incrementer

 

**4-bit Binary Incrementer**



# 1-4 Arithmetic Microoperations

## Binary Incrementer

- Binary Incrementer can also be implemented using a counter
- A binary decrements can be implemented by adding 1111 to the desired register each time!

- Register transfer microoperations
- Arithmetic microoperations (on numeric data stored in the registers)
- **Logic microoperations (bit manipulations on non-numeric data)**
- **Shift microoperations**

# 1-4 Arithmetic Microoperations

## Arithmetic Circuit

- This circuit performs **seven distinct arithmetic operations** and the basic component of it is the **parallel adder**
- The output of the binary adder is calculated from the following arithmetic sum:
  - $D = A + Y + C_{in}$

# 1-4 Arithmetic Microoperations

## Arithmetic Circuit <sup>cont.</sup>

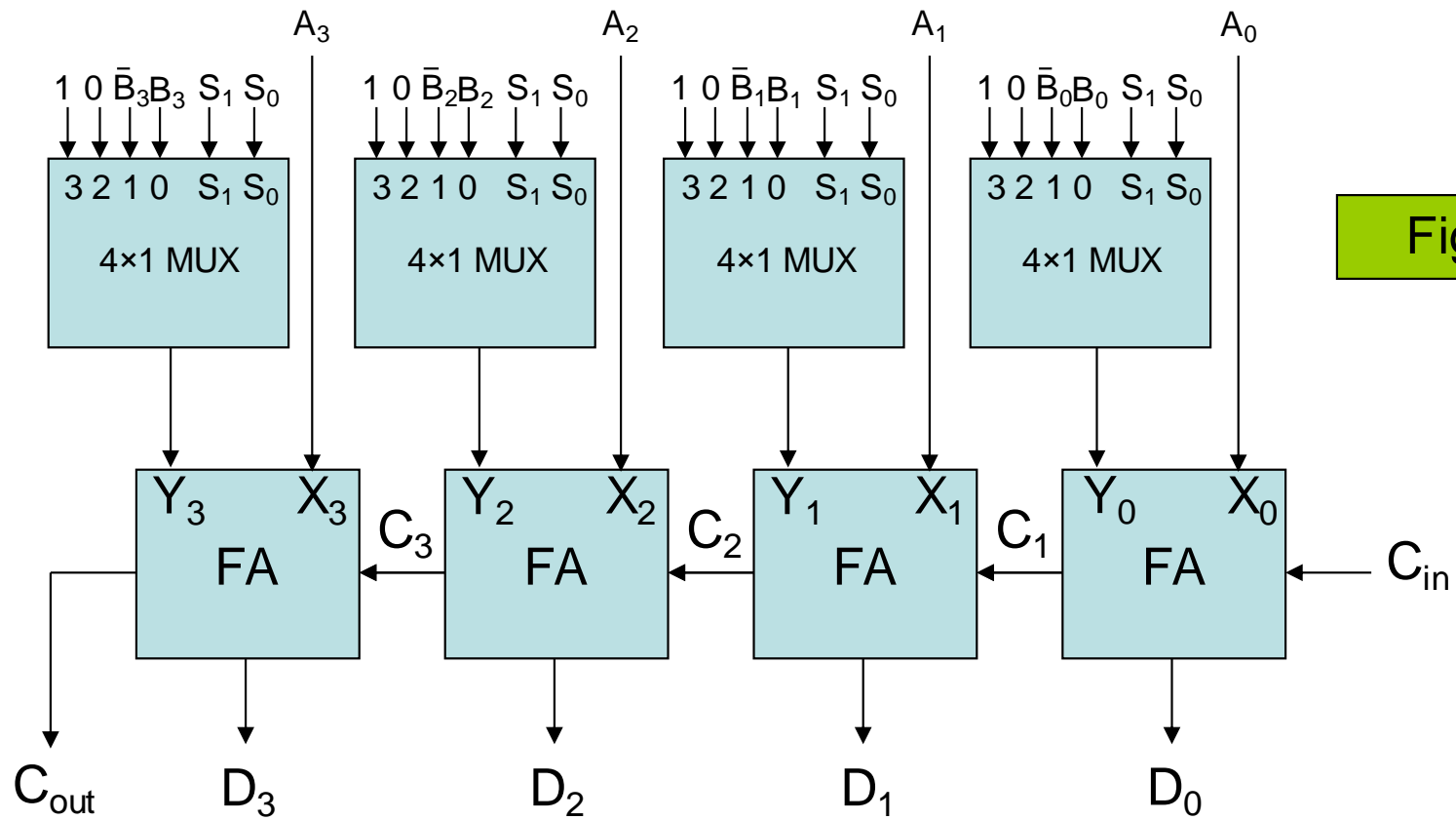


Figure A

**4-bit Arithmetic Circuit**

# 1-4 Arithmetic Microoperations

## Arithmetic Circuit <sup>cont.</sup>

Select			Input $Y$	Output $D = A + Y + C_{in}$	Microoperation
$S_1$	$S_0$	$C_{in}$			
0	0	0	$B$	$D = A + B$	Add
0	0	1	$B$	$D = A + B + 1$	Add with carry
0	1	0	$\overline{B}$	$D = A + \overline{B}$	Subtract with borrow
0	1	1	$\overline{B}$	$D = A + \overline{B} + 1$	Subtract
1	0	0	0	$D = A$	Transfer $A$
1	0	1	0	$D = A + 1$	Increment $A$
1	1	0	1	$D = A - 1$	Decrement $A$
1	1	1	1	$D = A$	Transfer $A$

# 1-5 Logic Microoperations


## The four basic microoperations

### OR Microoperation

- Symbol:  $\vee$ , +

- Gate: 

 - Example:  $100110_2 \vee 101011_2 = 101111_2$



# 1-5 Logic Microoperations

## The four basic microoperations

cont.

### AND Microoperation

- Symbol:  $\wedge$

- Gate: 

- Example:  $100110_2 \wedge 101011_2 = 100010_2$


# 1-5 Logic Microoperations

## The four basic microoperations

cont.

### Complement (NOT) Microoperation

- Symbol:  $\overline{\phantom{x}}$

 

- Gate:

- Example:  $\overline{1010110_2} = 0101001_2$




# 1-5 Logic Microoperations

## The four basic microoperations

cont.

### **XOR (Exclusive-OR) Microoperation**

- Symbol:  $\oplus$

 

- Gate:

- Example:  $100110_2 \oplus 101011_2 = 001101_2$

# 1-5 Logic Microoperations

## Other Logic Microoperations

### Selective-set Operation


- Used to force selected bits of a register into logic-1 by using the OR operation

- Example:  $0100_2 \vee 1000_2 = 1100_2$

In a processor register



Loaded into a register from  
memory to perform the  
selective-set operation



# 1-5 Logic Microoperations

## Other Logic Microoperations cont.

### Selective-complement (toggling) Operation

- Used to force selected bits of a register to be complemented by using the XOR operation

- Example:  $0001_2 \oplus 1000_2 = 1001_2$

In a processor register

Loaded into a register from  
memory to perform the  
selective-complement operation

# 1-5 Logic Microoperations

## Other Logic Microoperations cont.

### Insert Operation

- Step1: mask the desired bits
- Step2: OR them with the desired value
- Example: suppose  $R1 = 0110\ 1010$ , and we desire to replace the leftmost 4 bits (0110) with 1001 then:
  - Step1:  $0110\ 1010 \wedge 0000\ 1111$
  - Step2:  $0000\ 1010 \vee 1001\ 0000$
- $\rightarrow R1 = 1001\ 1010$


# 1-5 Logic Microoperations

## Other Logic Microoperations cont.

### NAND Microoperation

- Symbols:  $\wedge$  and  $\overline{\phantom{x}}$

- Gate:

 

- Example:  $\overline{100110_2 \wedge 101011_2} = 011101_2$


# 1-5 Logic Microoperations

## Other Logic Microoperations cont.

### NOR Microoperation

- Symbols:  $\vee$  and  $\overline{\phantom{x}}$

- Gate:

 

- Example:  $\overline{100110_2 \vee 101011_2} = 010000_2$

# 1-5 Logic Microoperations

## Other Logic Microoperations cont.

### **Set (Preset) Microoperation**

- Force all bits into 1's by ORing them with a value in which all its bits are being assigned to logic-1
- Example:  $100110_2 \vee 111111_2 = 111111_2$

### **Clear (Reset) Microoperation**

- Force all bits into 0's by ANDing them with a value in which all its bits are being assigned to logic-0
- Example:  $100110_2 \wedge 000000_2 = 000000_2$

# 1-5 Logic Microoperations


## Hardware Implementation

- The hardware implementation of logic microoperations requires that logic gates be inserted for each bit or pair of bits in the registers to perform the required logic function
- Most computers use only four (AND, OR, XOR, and NOT) from which all others can be derived.



# 1-5 Logic Microoperations
 
## Hardware Implementation <sup>cont.</sup>



$S_1$	$S_0$	Output	Operation
0	0	$E = A \oplus B$	XOR
0	1	$E = A \vee B$	OR
1	0	$E = A \wedge B$	AND
1	1	$E = A$	Complement


This is for one bit  $i$

Figure B

# 1-6 Shift Microoperations

- Used for serial transfer of data
- Also used in conjunction with arithmetic, logic, and other data-processing operations
- The contents of the register can be shifted to **the left** or to **the right**
- As being shifted, the first flip-flop receives its binary information from the serial input
- **Three types of shift: Logical, Circular, and Arithmetic**


# 1-6 Shift Microoperations cont.

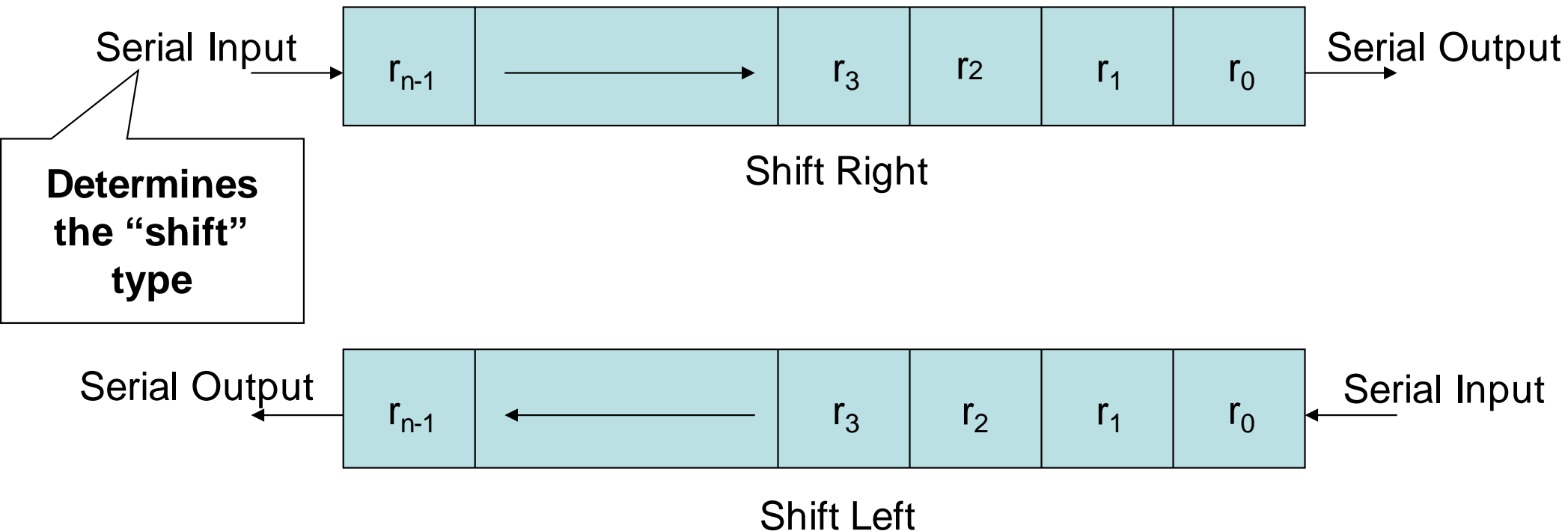

\*\*Note that the bit  $r_i$  is the bit at position (i) of the register

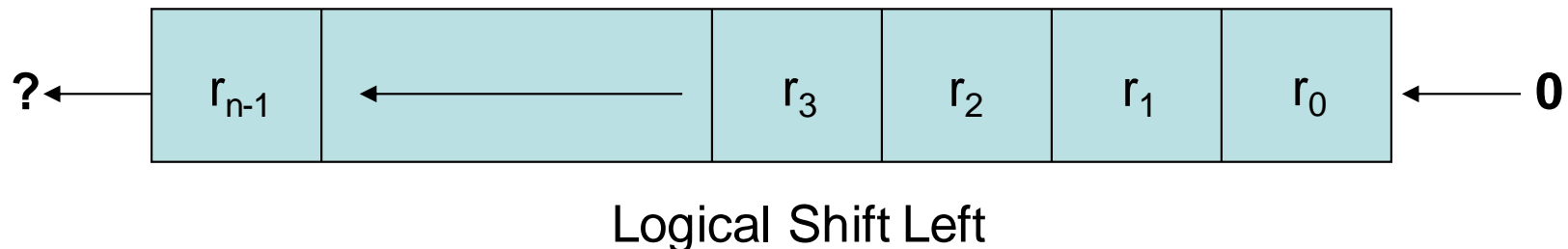
# 1-6 Shift Microoperations: Logical Shifts

- Transfers 0 through the serial input
- Logical Shift Right:  $R1 \leftarrow \text{shr } R1$   
The same
- Logical Shift Left:  $R2 \leftarrow \text{shl } R2$   
The same


 
# 1-6 Shift Microoperations: Circular Shifts (Rotate Operation)

- Circulates the bits of the register around the two ends without loss of information
- Circular Shift Right:  $R1 \leftarrow \text{cir } R1$   
The same
- Circular Shift Left:  $R2 \leftarrow \text{cil } R2$   
The same



Circular Shift Left



# 1-6 Shift Microoperations

## Arithmetic Shifts

- Shifts a signed binary number to the left or right
- An arithmetic shift-left multiplies a signed binary number by 2:    `ashl (00100): 01000`
- An arithmetic shift-right divides the number by 2  
    `ashr (00100) : 00010`
- An overflow may occur in arithmetic shift-left, and occurs when the sign bit is changed (sign reversal)

# 1-6 Shift Microoperations

## Arithmetic Shifts <sup>cont.</sup>

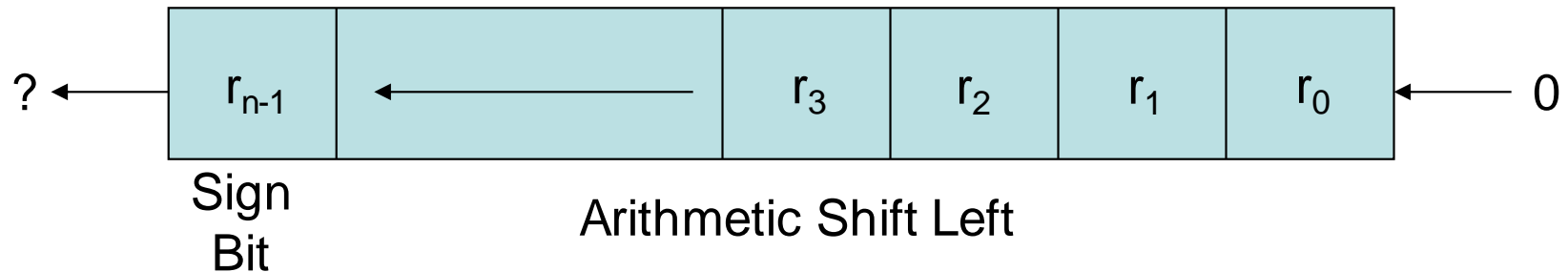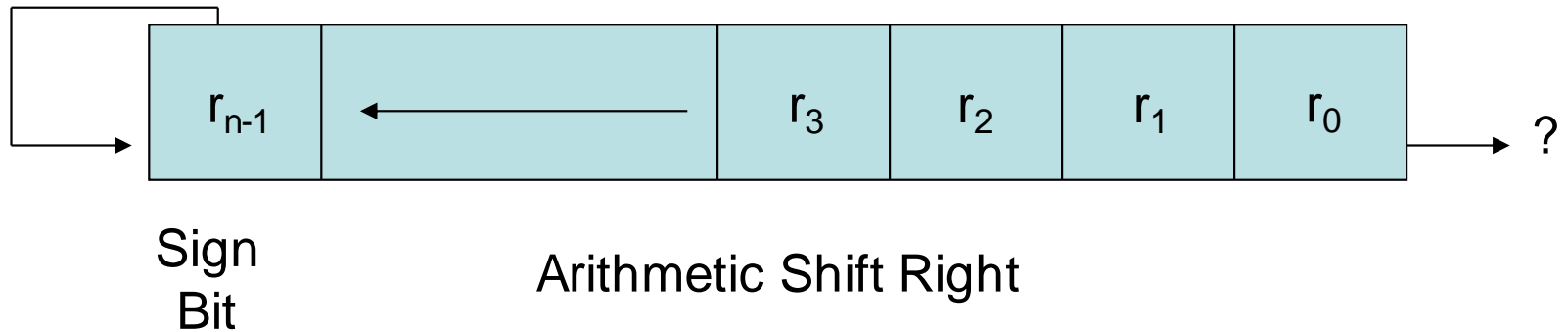


# 1-6 Shift Microoperations

## Arithmetic Shifts <sup>cont.</sup>

- An overflow flip-flop  $V_s$  can be used to detect an arithmetic shift-left overflow

$$V_s = R_{n-1} \oplus R_{n-2}$$

 



# 1-6 Shift Microoperations <sup>cont.</sup>

- Example: Assume  $R1 = 11001110$ , then:
  - Arithmetic shift right once :  $R1 = 11100111$
  - Arithmetic shift right twice :  $R1 = 11110011$
  - Arithmetic shift left once :  $R1 = 10011100$
  - Arithmetic shift left twice :  $R1 = 00111000$
  - Logical shift right once :  $R1 = 01100111$
  - Logical shift left once :  $R1 = 10011100$
  - Circular shift right once :  $R1 = 01100111$
  - Circular shift left once :  $R1 = 10011101$


# 1-6 Shift Microoperations

## Hardware Implementation <sup>cont.</sup>

- A possible choice for a shift unit would be a bidirectional shift register with parallel load has drawbacks:
  - **Needs two pulses (the clock and the shift signal pulse)**
  - **Not efficient in a processor unit where multiple number of registers share a common bus**
- It is more efficient to implement the shift operation with a combinational circuit

# 1-6 Shift Microoperations

## Hardware Implementation cont.

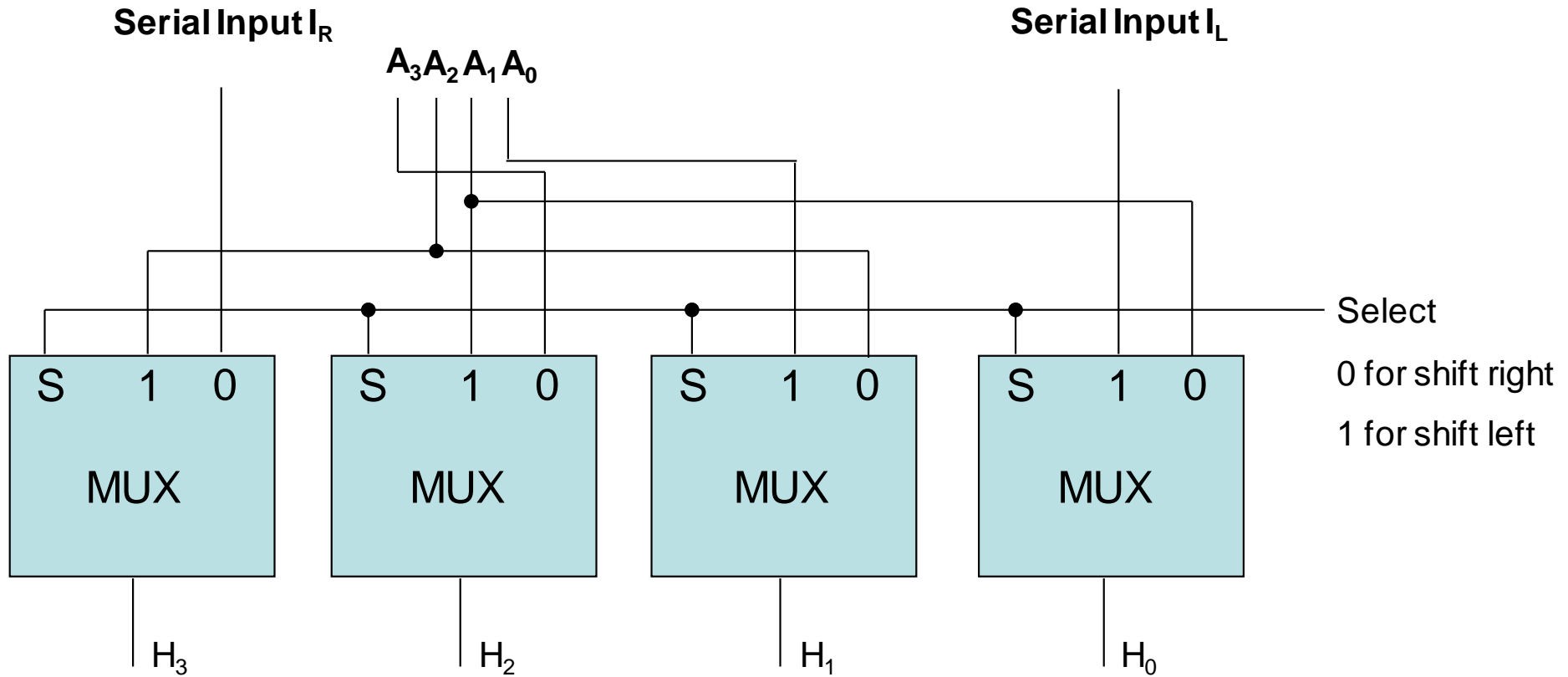

**4-bit Combinational Circuit Shifter**

# 1-7 Arithmetic Logic Shift Unit

- Instead of having individual registers performing the microoperations directly, computer systems employ a number of storage registers connected to a common operational unit called an Arithmetic Logic Unit (**ALU**)

# 1-7 Arithmetic Logic Shift Unit cont.

